

**Solution to Problem No. 36:**

In the above problem, the total number of capacitor plates are  $n$ , so the total number of capacitors in series are  $(n - 1)$ .

For the first capacitor with plate areas  $A$  and  $A/2$ , the effective area for this capacitor will be taken to be  $A/2$ , that of  $A/2$  and  $A/4$ , the effective capacitor area will be  $A/4$  and so on.

All the capacitor plates are connected in series.

For the effective capacitance in series, we have the general formula:

$$1/C_{\text{effective}} = 1/C_1 + 1/C_2 + 1/C_3 + \dots + 1/C_n$$

For each capacitor of plate area  $A$  and plate separation  $d$ , we have the general capacitance formula as  $C = \epsilon_0 A/d$  where  $\epsilon_0$  is called the permittivity constant whose value is  $8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$ .

(a)

Hence for the given system we have

$$1/C_{\text{effective}} = d/\epsilon_0(A/2) + d/\epsilon_0(A/4) + \dots + d/\epsilon_0(A/2^{n-1})$$

$$1/C_{\text{effective}} = \{d/\epsilon_0 A\}\{2 + 2^2 + 2^3 + \dots + 2^{n-1}\}$$

The above expression contains a geometric progression with  $(n - 1)$  terms. Using the formula of geometric equation to it, we get

$$1/C_{\text{effective}} = \{d/\epsilon_0 A\}\{2\}\{2^{n-1} - 1\}$$

Hence the effective capacitance is

$$C_{\text{effective}} = \{\epsilon_0 A/d\}/\{2^n - 2\} \dots \dots \dots \text{ANSWER}$$

(b)

For the second part, we first calculate the effective capacitance of the combination.

$$1/C_{\text{effective}} = d/k\epsilon_0(A/2) + d/\epsilon_0(A/4) + \dots + d/\epsilon_0(A/2^{n-1})$$

$$1/C_{\text{effective}} = 2d/k\epsilon_0 A + 4 d/\epsilon_0 A + \dots + 2^{n-1}d/\epsilon_0 A$$

Taking the factor  $2$  common from the second expression, we get

$$1/C_{\text{effective}} = 2d/k\epsilon_0 A + \{2d/\epsilon_0 A\}\{2 + 2^2 + 2^3 + \dots + 2^{n-2}\}$$

The second expression again consists of a GP but with  $(n - 2)$  terms. Hence applying the formula for sum of a geometric progression and taking the factor  $\{2d/\epsilon_0 A\}$  common, we get

$$1/C_{\text{effective}} = \{2d/\epsilon_0 A\}\{(1/k) + 2(2^{n-2} - 1)\}$$

$$1/C_{\text{effective}} = \{2d/k\epsilon_0 A\}\{1 + k(2^{n-1} - 2)\}$$

Hence,

$$C_{\text{effective}} = \{k\epsilon_0 A/2d\}\{1/[1 + k(2^{n-1} - 2)]\}$$

Also, if  $Q$  is the charge stored in the system when emf  $E$  is applied across the assembly, then the charge is given by

$$Q = EC_{\text{effective}}$$

Hence the charge stored in the capacitor combination in the second case is

$$Q = \{k\epsilon_0 AE/2d\}\{1/[1 + k(2^{n-1} - 2)]\} \dots \dots \dots \text{ANSWER}$$

Solution by  
 Royan John D'Mello  
 XII Pass, St.Aloysius PU College, Mangalore